

Capacitance (II)


Text sections 26.3–26.5

- Capacitors in circuits


Practice: chapter 26,
Objective Questions 1, 8, 11
Conceptual Question 8
Problems 15, 19, 25, 35, 38, 48, 49

Capacitors in Circuits


Symbols:

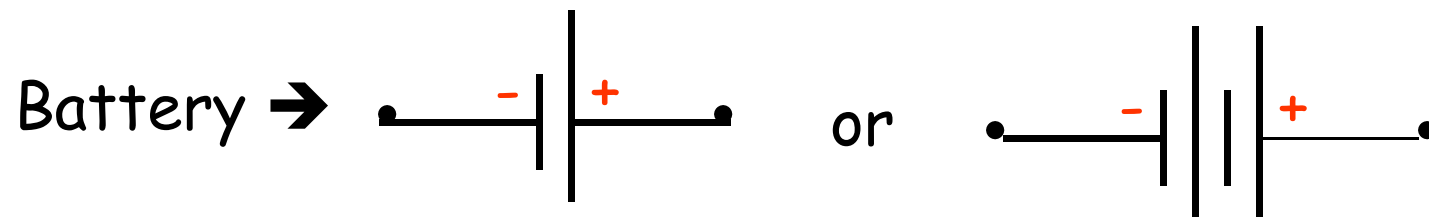

Capacitor Combinations

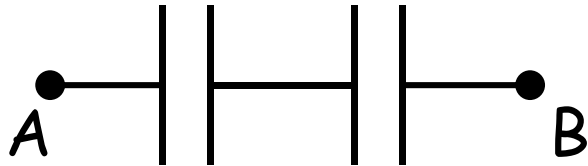

Series

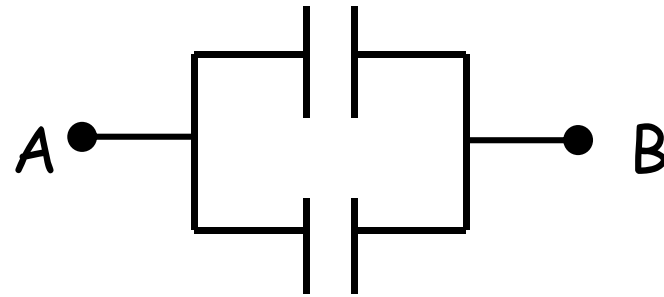


Parallel

What is the "effective capacitance" between A & B?



$$C_{eff} = \frac{\text{charge transferred}}{\text{voltage produced}}$$

Parallel

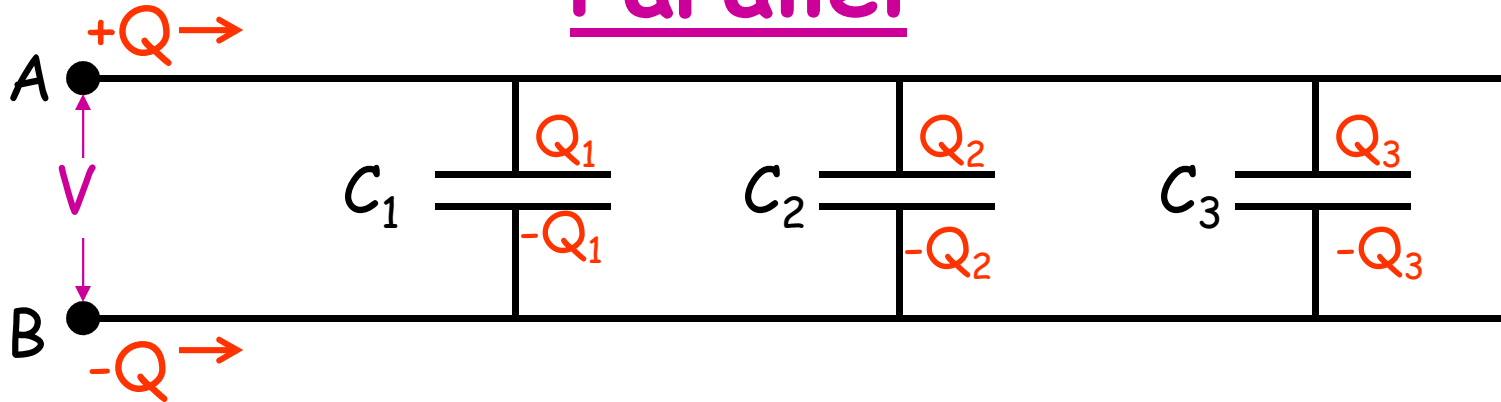


Voltages are the same: $V_1 = V_2 = V_3 = \dots = V$

Charges add: $Q_1 + Q_2 + Q_3 + \dots = Q$

But... $Q_1 = C_1V$, $Q_2 = C_2V$, ...

$$\Rightarrow C_{eff} = C_1 + C_2 + \dots$$

Series

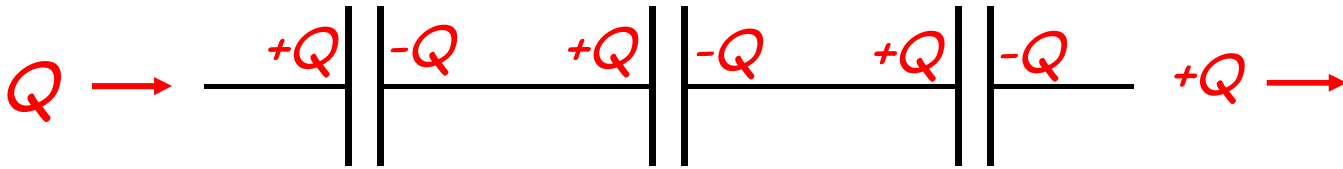

Voltages add: $V_1 + V_2 + \dots = V$


Charges are equal: $Q_1 = Q_2 = Q_3 = Q$

$$\text{And ... } V = \frac{Q}{C_{eff}}, \quad V_1 = \frac{Q_1}{C_1} = \frac{Q}{C_1}, \quad \dots$$


$$\Rightarrow \frac{1}{C_{eff}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$


Example

Find the capacitance between a and b.

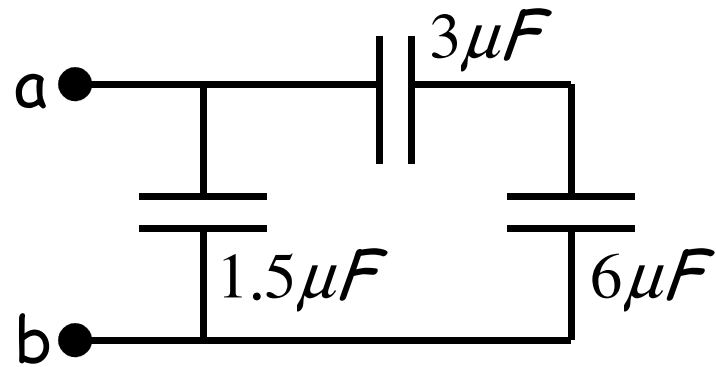


Solution:

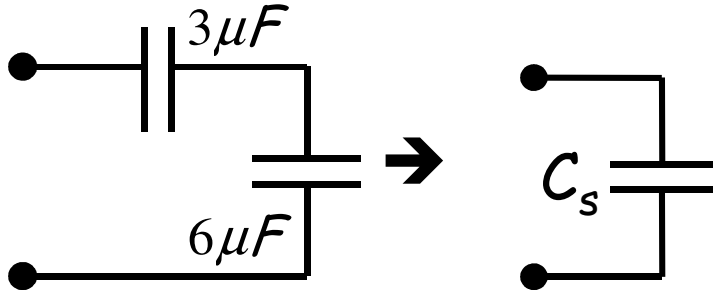(1)  $C_s = \frac{1}{\left(\frac{1}{3} + \frac{1}{6}\right)} \mu F = 2 \mu F$

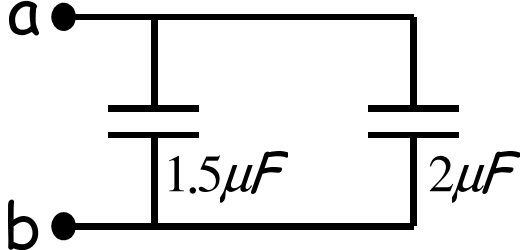(2)  $C_{ab} = 2 + 1.5$
 $= \underline{\underline{3.5 \mu F}}$

Quiz

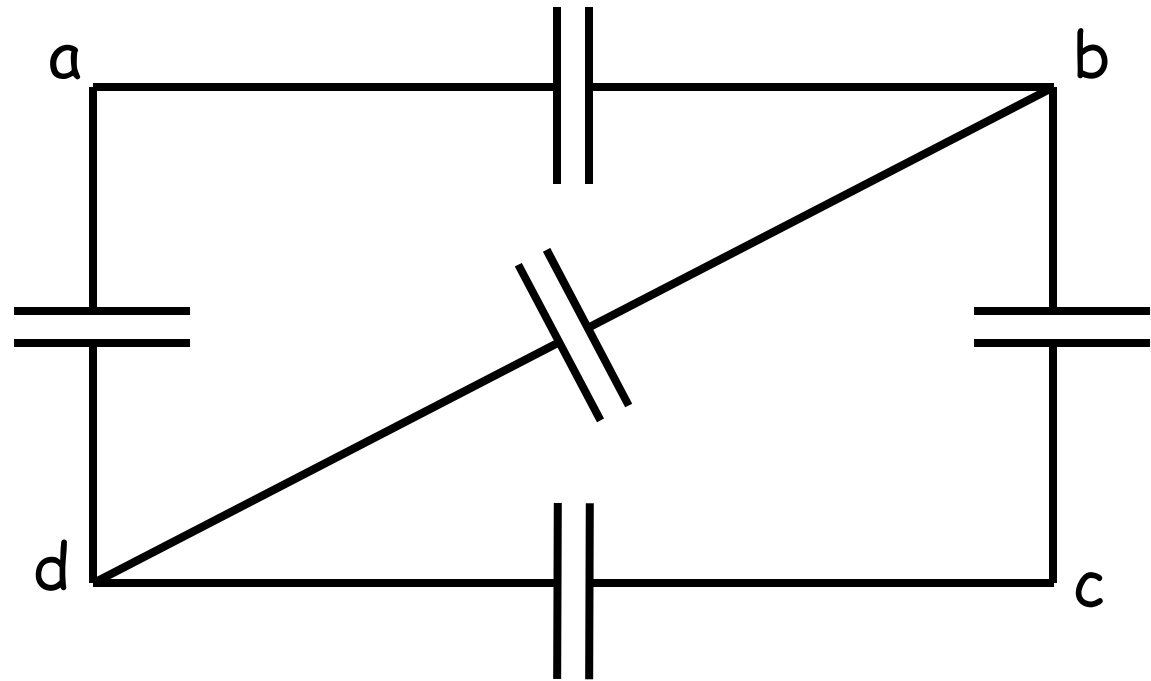


All Capacitors are $12\mu F$

The capacitance between points b and d is

- A) $12\mu F$ B) $6\mu F$ C) $2.4\mu F$ D) $24\mu F$ E) $60\mu F$


Exercise

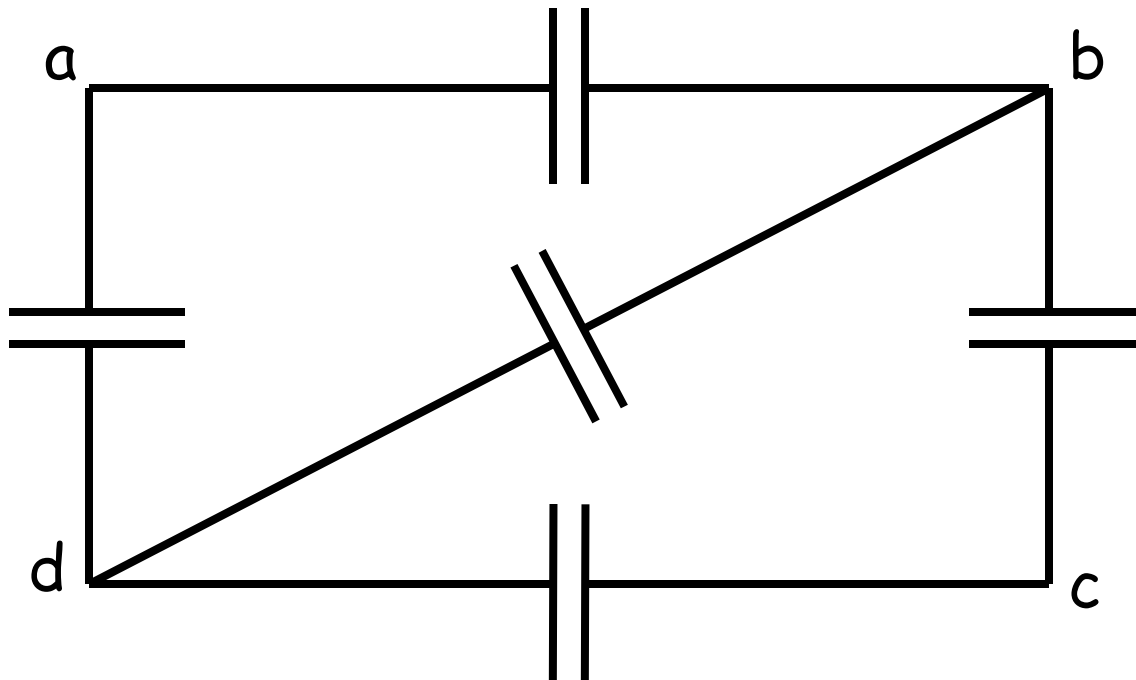

All Capacitors are $12\mu F$

Find the capacitance between points a and d.


Quiz

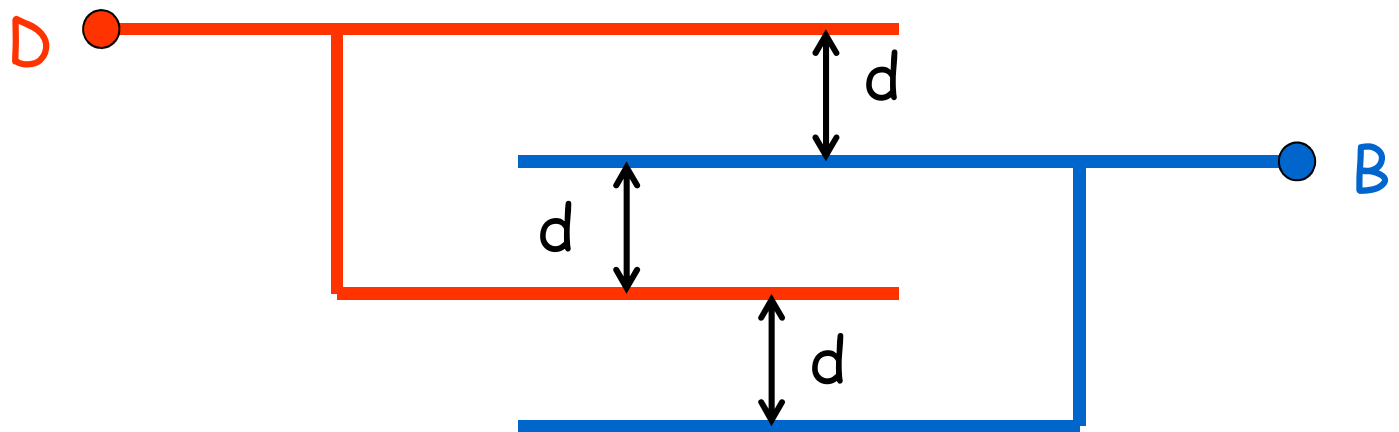

4 plates, each of area A , are connected as shown.
What is the capacitance between B and D?

- A) $\frac{1}{2} \epsilon_0 A/d$
- B) $\frac{1}{4} \epsilon_0 A/d$
- C) $\frac{1}{3} \epsilon_0 A/d$
- D) $3 \epsilon_0 A/d$
- E) $4 \epsilon_0 A/d$

Energy Stored in a Capacitor

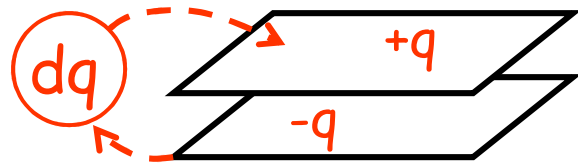

Remove dq from lower plate and add to upper plate:

Increase in P.E., $dU = Vdq = \frac{q}{C} dq$

Start at $q = 0$, finish at $q = Q$: $U = \int_0^Q \frac{q}{C} dq = \frac{Q^2}{2C}$

$$\Rightarrow U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} QV = \frac{1}{2} CV^2$$

We can think of this energy as *stored in the electric field* set up when the capacitor is charged:

Parallel-Plate Capacitor: $C = \frac{\epsilon_0 A}{d}$ and $V = E \cdot d$

$$\Rightarrow U = \frac{1}{2} CV^2 = \frac{1}{2} \epsilon_0 E^2 \cdot \underbrace{(Ad)}_{\text{Volume between plates}}$$


"Energy density"

$$u_E = \frac{U}{\text{volume}} = \frac{1}{2} \epsilon_0 |\mathbf{E}|^2$$

(Units: J/m³)

This also applies to *any* electric field.

Quiz

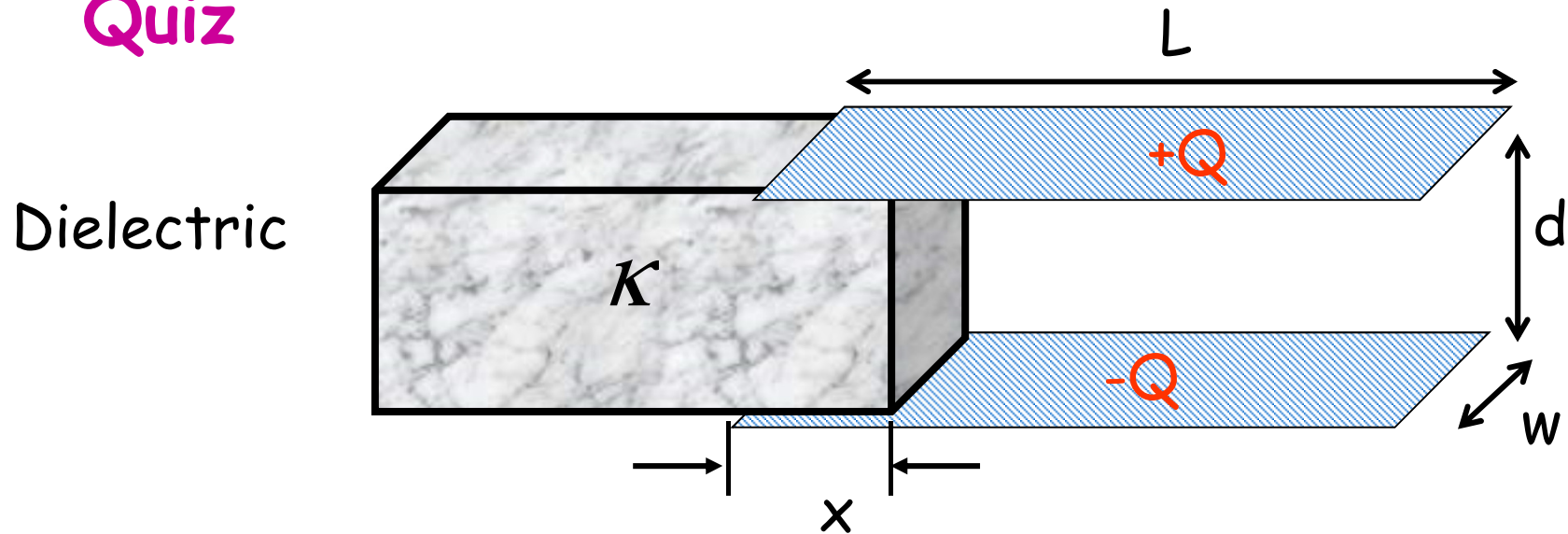

A dielectric is slid into the space between the plates of a charged capacitor. What happens?

- A) The energy stored in the capacitor increases
- B) The energy stored in the capacitor decreases
- C) No change




What is the direction of the electrostatic force on the dielectric?

What is the magnitude of this force?

Quiz

Conducting spheres and a long wire:

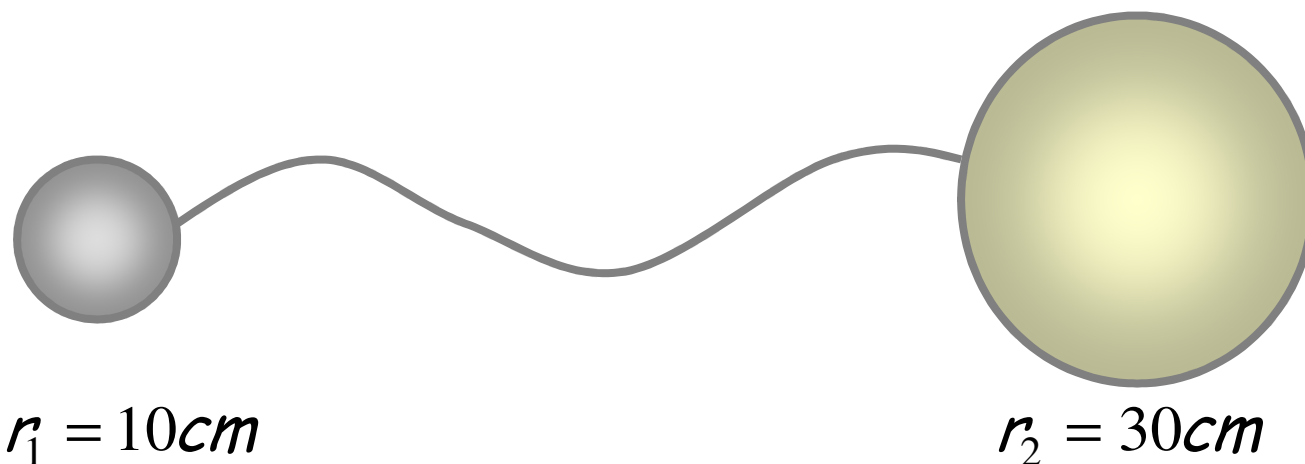

A total charge $+12\ \mu\text{C}$ is placed on one sphere. Some of the charge will move to the other sphere until

- A) the electric fields outside the spheres are equal
- B) the electric potentials on the spheres are equal
- C) the electric charges on the spheres are equal
- D) all of the above