

Kirchhoff's Circuit Rules

Text section 28.3

Kirchhoff's circuit rules


*Practice: Chapter 28,
Objective Question 12
Problems 31, 57, 66, 73*

Kirchhoff's Circuit Rules

Junction Rule: total current in = total current out at each junction (*from conservation of charge*).


Loop Rule: Sum of *emfs* and *potential differences* around any closed loop is zero (*from conservation of energy*).

Junction Rule: conservation of charge.

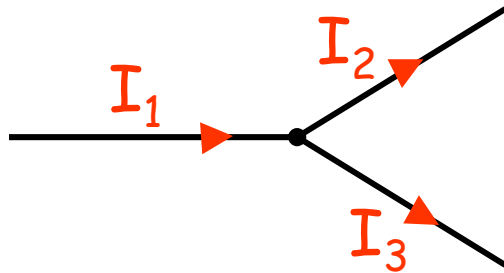

$$I_1 = I_2 + I_3$$

or

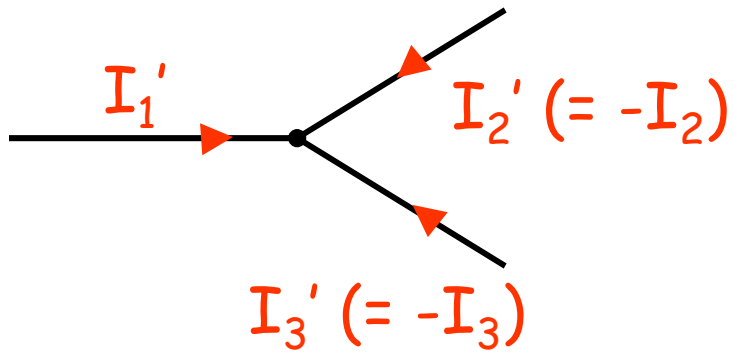

$$I_1' + I_2' + I_3' = 0$$

Loop Rule: conservation of energy.

Follow a test charge q around a loop:


→ $\sum q \times (\Delta V_i) = 0$ around any loop in circuit.




$$\Delta V = -IR$$



$$\Delta V = +IR$$

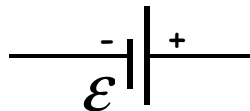


$$\Delta V = \mathcal{E}$$

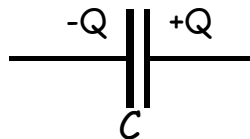

$$\Delta V = Q/C$$

changes going from left to right

Example

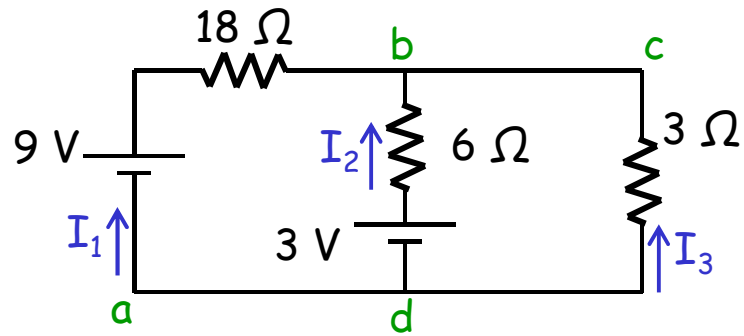


Find the current through each battery.

Quiz


The junction rule will give:

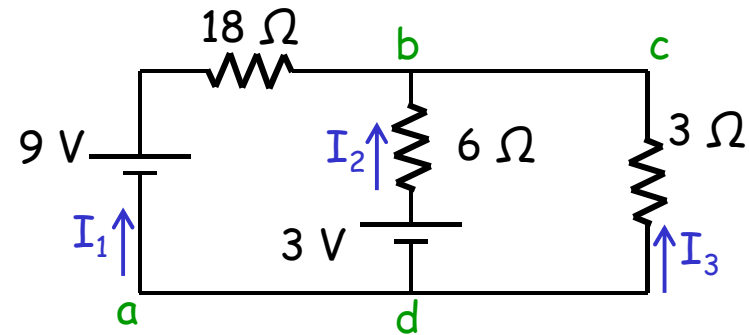- A) $I_1 + I_2 + I_3 = 0$
- B) $-I_1 + I_2 + I_3 = 0$
- C) $I_1 - I_2 + I_3 = 0$
- D) $I_1 + I_2 - I_3 = 0$
- E) none of these



Quiz

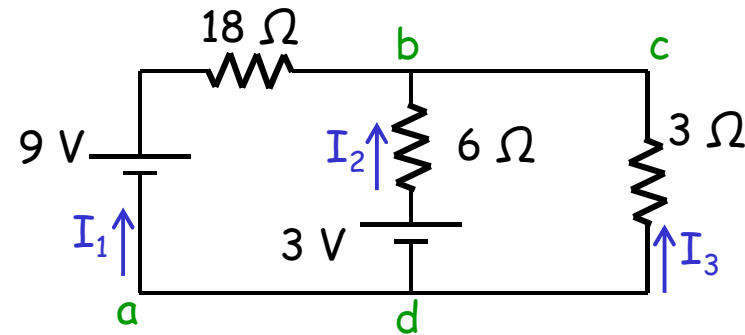
The loop rule applied to loop *abcd* will give:



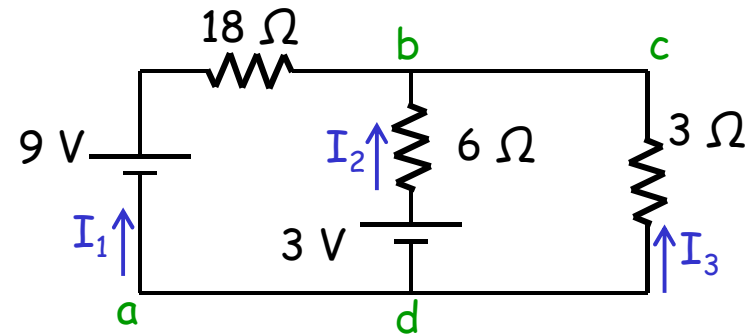- A) $9A - 18I_1 - 3I_3 = 0$
- B) $9A + 18I_1 - 3I_3 = 0$
- C) $9A + 18I_1 + 3I_3 = 0$
- D) $9A - 18I_1 + 3I_3 = 0$
- E) none of these


Quiz

The loop rule applied to loop *abda* will give:



- A) $12A - 18I_1 + 6I_2 = 0$
- B) $12A - 18I_1 - 6I_2 = 0$
- C) $6A - 18I_1 - 6I_2 = 0$
- D) $6A + 18I_1 + 6I_2 = 0$
- E) $6A - 18I_1 + 6I_2 = 0$

Exercise

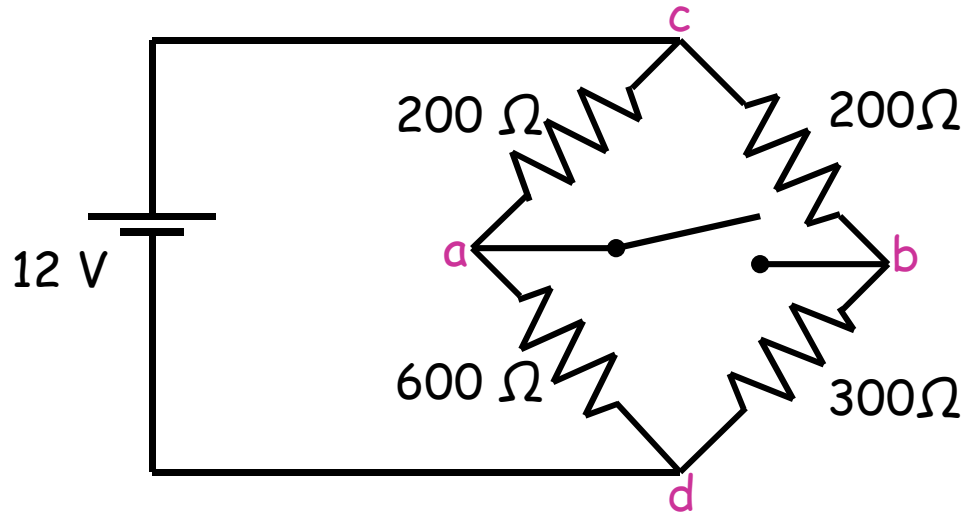


What is V_{ab} (i.e., $V_a - V_b$) when the switch is open?

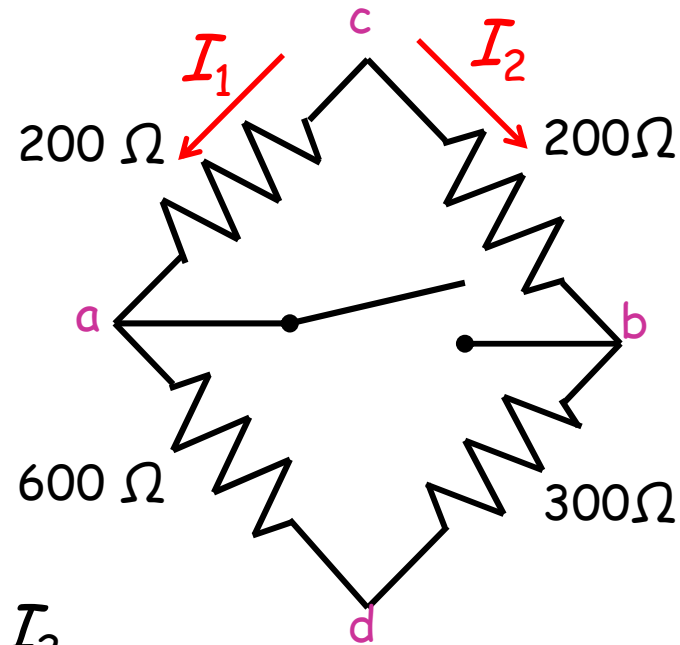Exercise for fun: Find the current through the switch when it is closed.


Quiz:

The loop rule requires that V_{ab} (i.e., $V_a - V_b$) should obey:



- A) $V_{ab} = (200\ \Omega)I_1 + (200\ \Omega)I_2$
- B) $V_{ab} = (200\ \Omega)I_1 - (200\ \Omega)I_2$
- C) $V_{ab} = -(200\ \Omega)I_1 + (200\ \Omega)I_2$
- D) $V_{ab} = -(200\ \Omega)I_1 - (200\ \Omega)I_2$


Example: Effective resistance

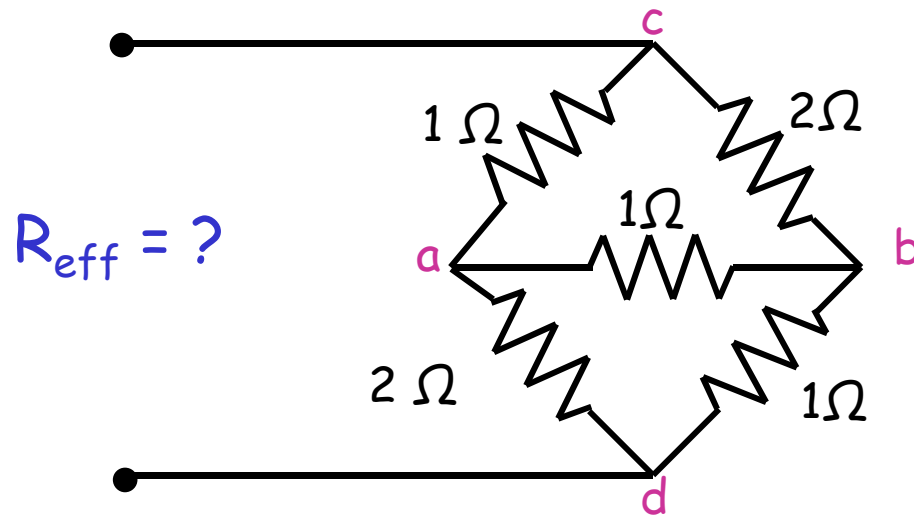

"Series and parallel" rules don't help in this case. You have to go back to the fundamentals—Kirchhoff's Circuit Rules.

(Answer: $R_{\text{eff}} = 1.4\ \Omega$)

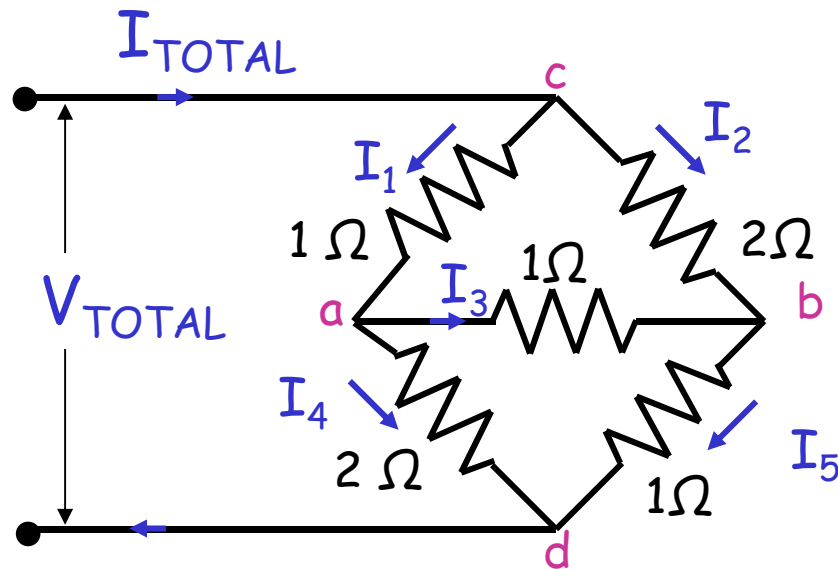Solution plan: $R_{\text{eff}} = V_{\text{TOTAL}}/I_{\text{TOTAL}}$



Show that:

$$I_1 = I_5 = 3I_3$$

$$I_2 = I_4 = 2I_3$$

$$I_{\text{TOTAL}} = 5I_3$$

$$V_{\text{TOTAL}} = (7\ \Omega) I_3$$

- 1) Use Kirchhoff's rules to write everything in terms of one variable (e.g., I_3).
- 2) Divide $V_{\text{TOTAL}}/I_{\text{TOTAL}}$.