

Inductance (II)

Text sections 32.2

- Inductors in circuits
- RL circuits

Practice:

Chapter 32,

Objective Questions 4, 7

Conceptual Questions 3, 4, 5

Problems 19, 21, 22, 31

Self-Inductance

$$\mathcal{E}_L = -L \frac{dI}{dt}$$




*Potential energy stored
in an inductor:*

$$U_L = \frac{1}{2} LI^2$$

*Energy density in a
magnetic field:*

$$u_B \equiv \frac{U}{\text{Volume}} = \frac{B^2}{2\mu_0}$$

Example:

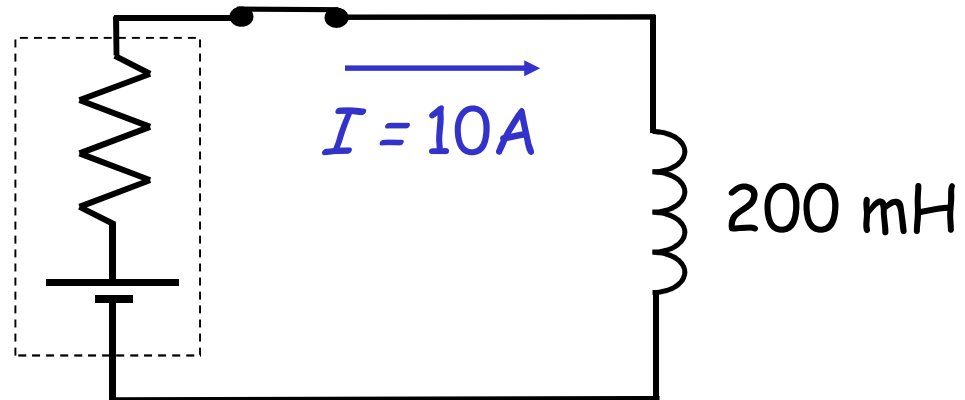


Initial: $I_i = 10A$, $U_i = \frac{1}{2} (0.2 \text{ H})(10 \text{ A})^2$
 $= 10\text{J}$

Final: $I_f = 0$, $U_f = 0\text{J}$ (after switch is opened)

Where does the energy go?


Example:

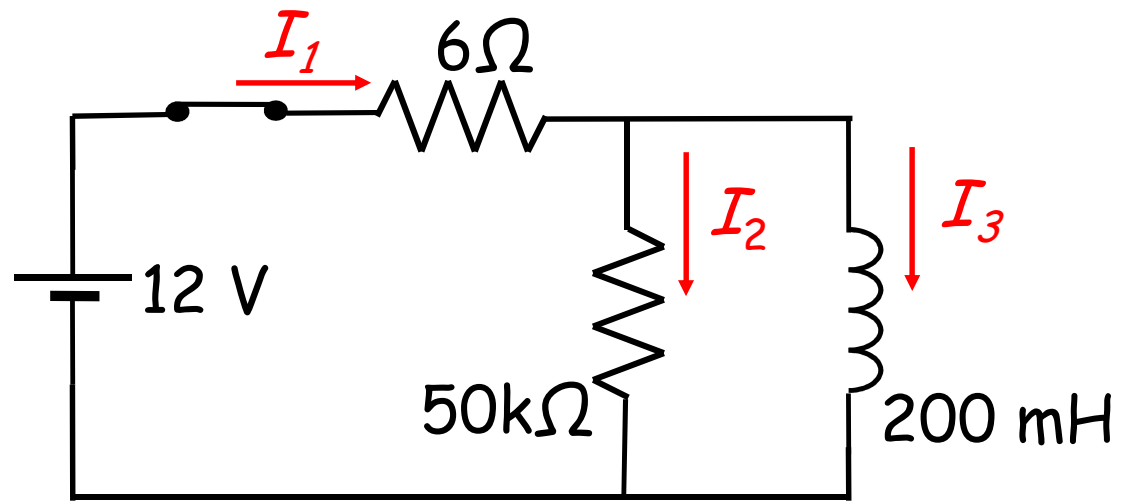

- The switch has been closed for a long time. Find the current through each component, and the voltage across each component.*
- The switch is now opened. Find the currents and voltages just afterwards.*
- How long does it take for the inductor current to drop to zero (after the switch is opened)?*


Quiz

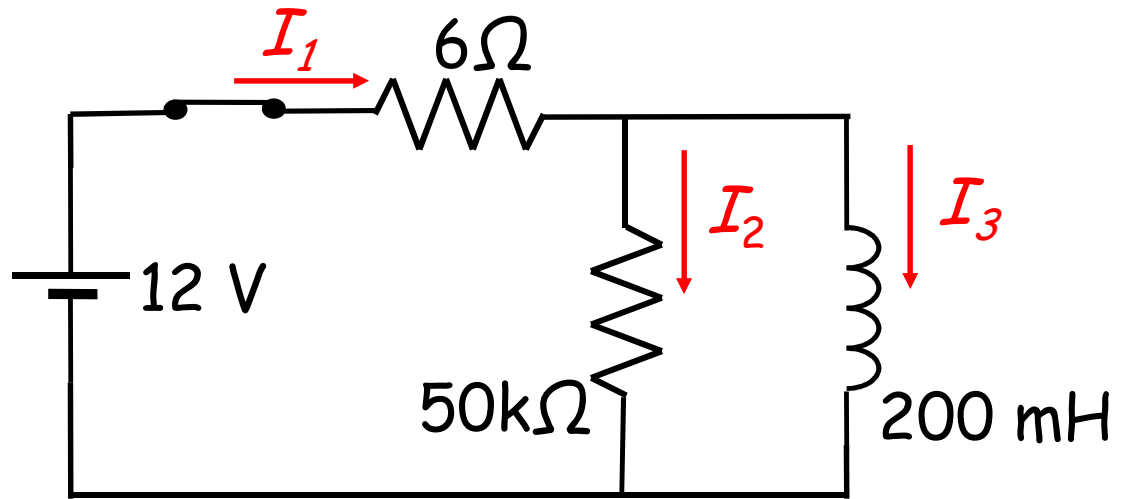The switch has been closed for a long time. Which currents are zero?



- A) I_1
- B) I_2
- C) I_3
- D) All of them
- E) None of them

Quiz

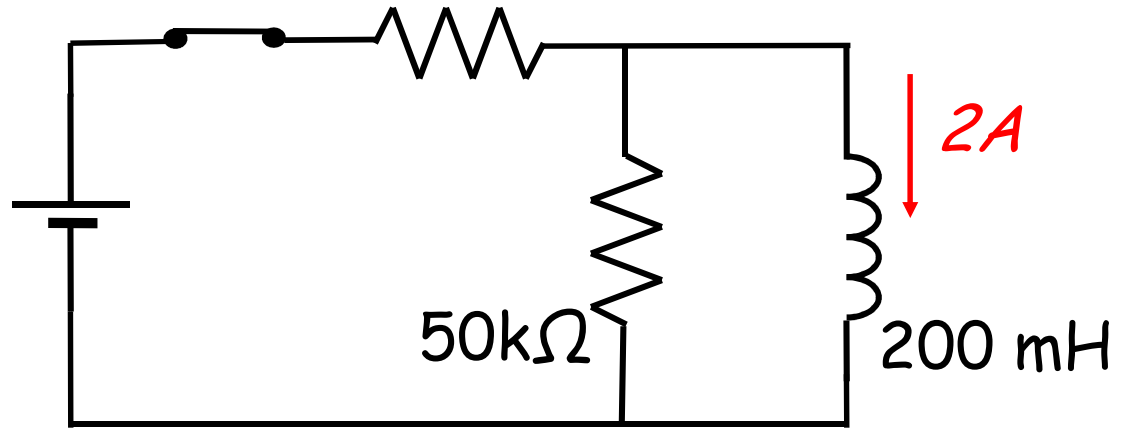


There is a 2A current through the inductor, and the switch is suddenly opened. What is the voltage across the inductor immediately after the switch is opened?

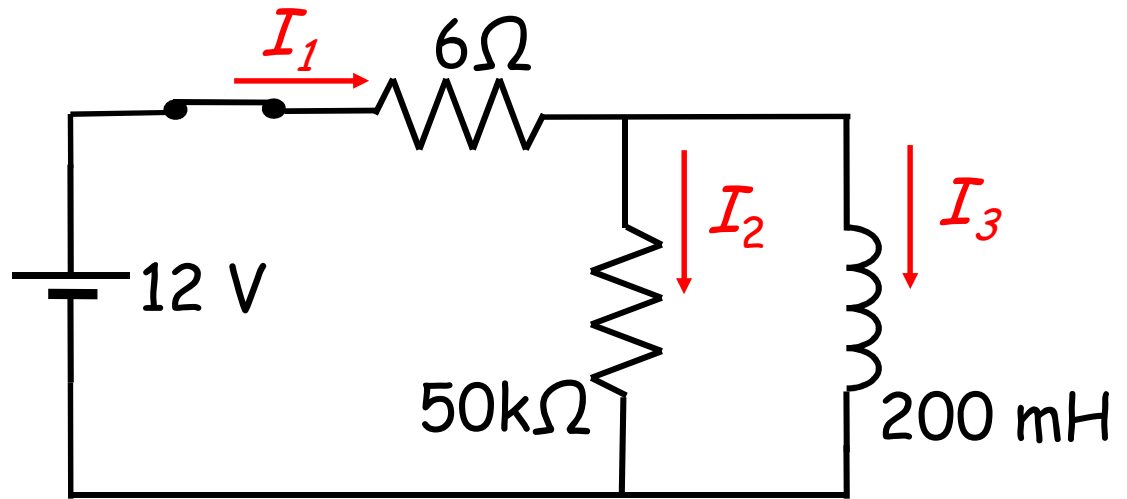- A) 12 V
- B) 100kV
- C) zero
- D) 10V

Quiz


Suppose the switch had been open for a long time. What is the current I_2 just after it is closed?



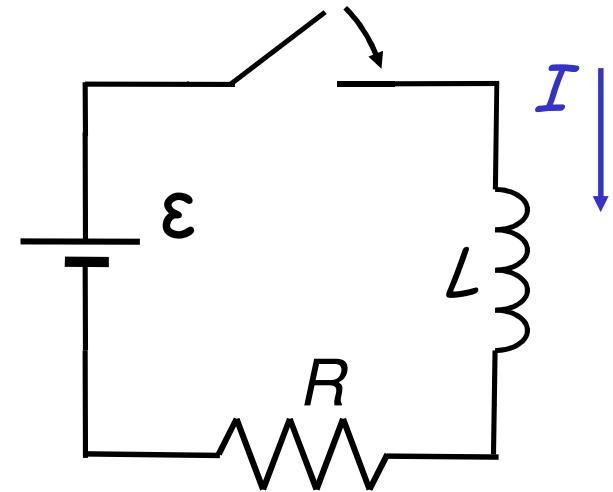- A) 2.0 A
- B) 0.24 mA
- C) zero

RL circuits: time dependence

*The switch is closed at $t = 0$;
Find $I(t)$.*



Kirchhoff's loop rule:

$$\varepsilon - L \frac{dI}{dt} - IR = 0$$

$$\Rightarrow \frac{dI}{dt} = \frac{\varepsilon - IR}{L} = \frac{R}{L} \left(\frac{\varepsilon}{R} - I \right)$$

separate the variables: $\frac{dI}{(\varepsilon/R) - I} = \frac{R}{L} dt$

Integrate from time zero to time t , or zero current to current $I(t)$:

$$\int_0^{I(t)} \frac{dI}{(\mathcal{E}/R) - I} = \int_0^t \frac{R}{L} dt$$

But, $\int \frac{dx}{a-x} = -\ln(a-x)$

So $-\ln\left(\frac{\mathcal{E}}{R} - I(t)\right) + \ln\left(\frac{\mathcal{E}}{R} - 0\right) = \frac{R}{L}t$

and with a little work,

$$I = \frac{\mathcal{E}}{R} \left(1 - e^{-(R/L)t}\right)$$

Time Constant:



$$\tau = \frac{L}{R}$$

note $H/\Omega = \text{seconds}$
(exercise!)

Time Constant: $\tau = \frac{L}{R}$


Close switch at $t = 0$:
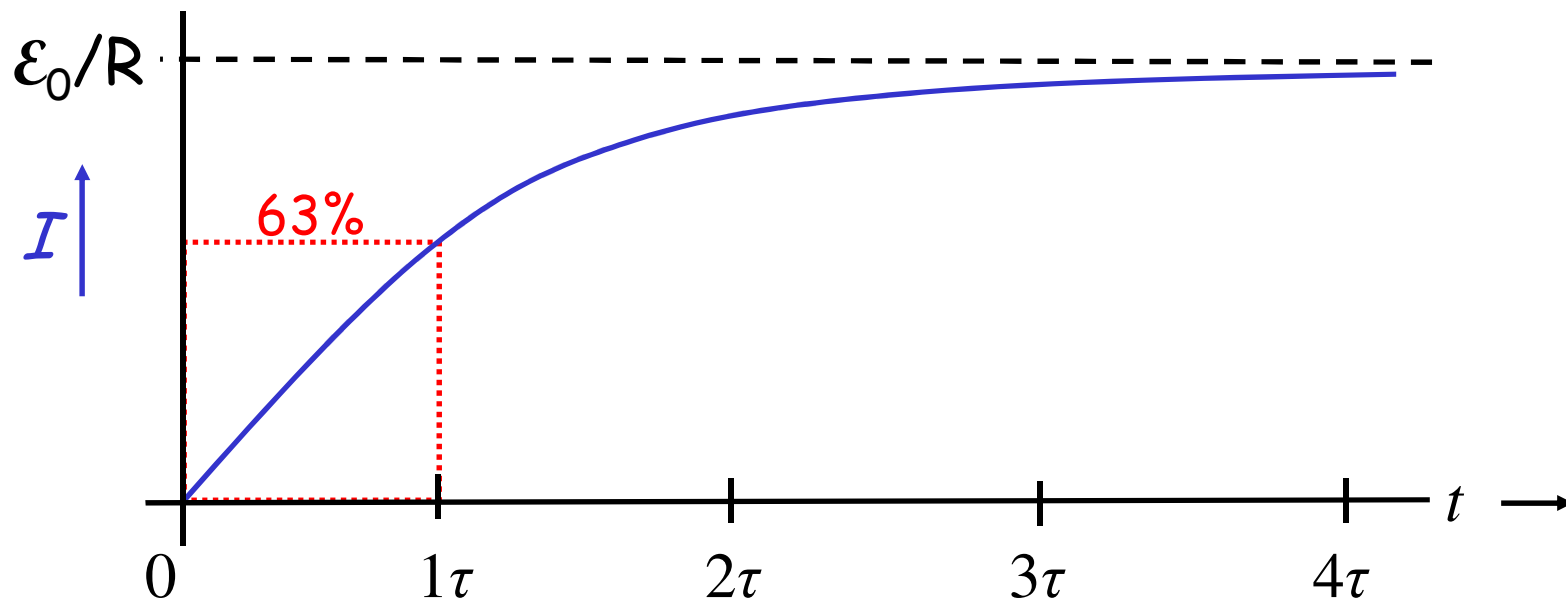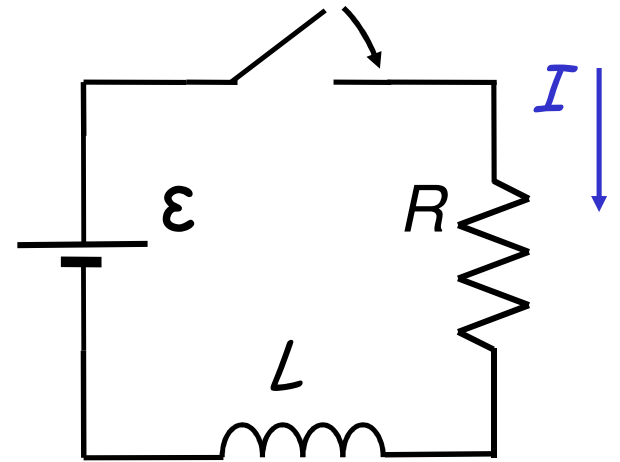
$$I(t) = \frac{\mathcal{E}}{R} \left(1 - e^{-t/\tau} \right)$$




Current decreasing:


Time Constant: $\tau = \frac{L}{R}$

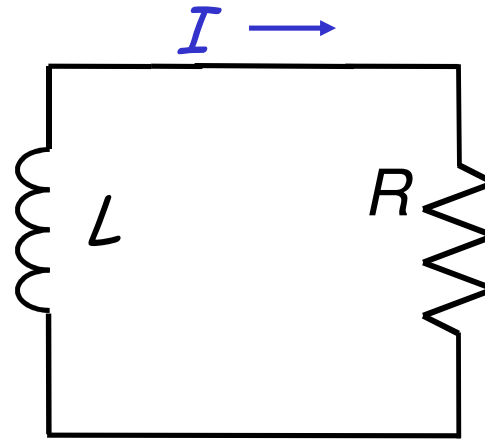

$$I(t) = I_0 \left(e^{-t/\tau} \right)$$

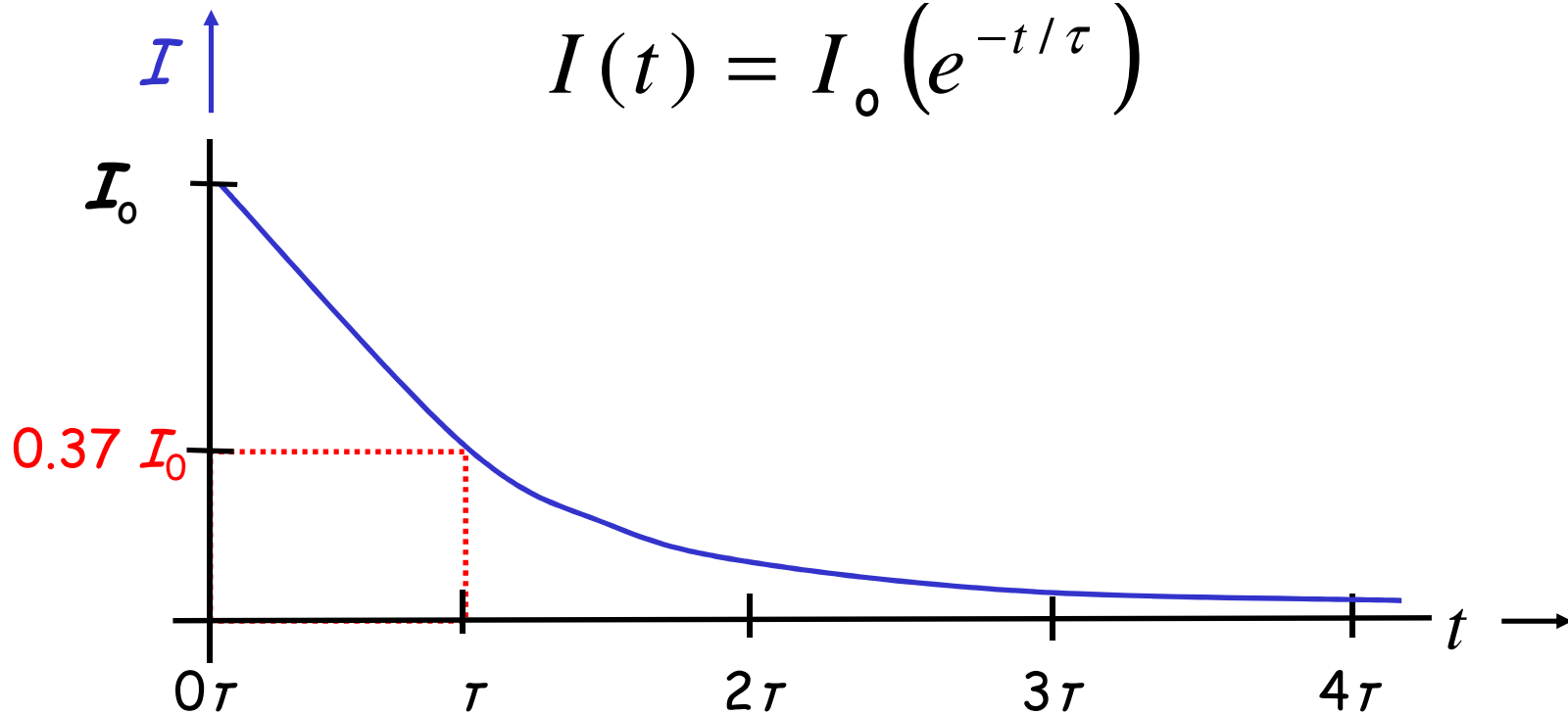

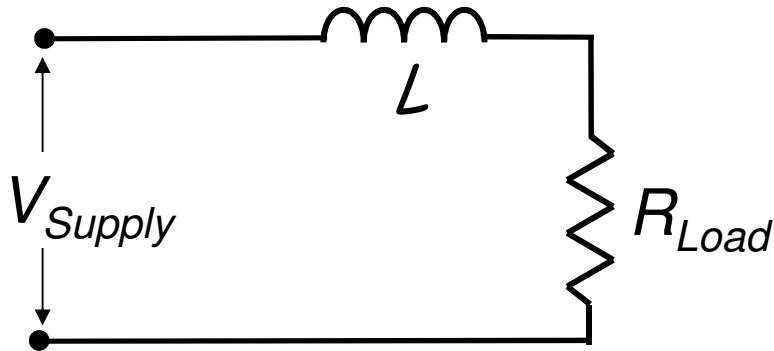Inductor application: *Filtering voltage spikes*



$$R_{Load} = 10 \Omega$$

$$L = 0.5 \text{ H}$$

$$V_{Supply} = 10 \text{ volts}$$

What is the steady-state voltage across R_{Load} ?

What is the maximum voltage across R_{Load} if the supply voltage is increased to 100 volts for 1 millisecond?

